

RESISTANCE-INDUCTANCE AND RESISTANCE-CAPACITANCE FILTER CIRCUITS
PREPARATORY WORK

1. Explain the operation of low pass filter circuits.
2. Explain the operation of high-pass filter circuits.
3. Obtain the expressions for the corner frequency of R-L and R-C filters
4. Describe the experimental calculation of the corner frequency in R-L and R-C filters.

NOTE: Come to the experiments by preparing the preparatory work as a report (with the report cover). Those without a preparation report will not be admitted to the experiments.

HIGH-FREQUENCY LOW-FREQUENCY FILTERS

Series RC and RL circuits are often used as filters. They act as a high-frequency filter by attenuating low-frequency components while passing high-frequency components, and as a low-frequency filter by attenuating high-frequency signals while passing low-frequency components.

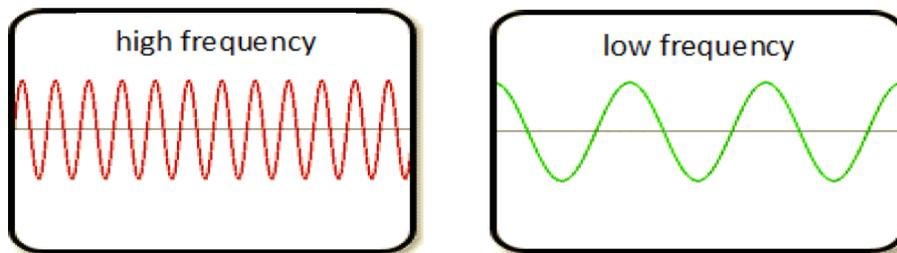


Figure 1. High and low frequency signals

For various circuits (such as amplifiers and filters) the frequency dependence of the input/output ratios can be easily seen. $\left[\frac{(V_p)_o}{(V_p)_i} \right]$ value, in “decibels, DB”, gives the gain of an amplifier or filter.

High-Frequency RC Filters

Figure 2 shows how a series RC circuit must be connected to work as a high-frequency filter. In each case, the input and output are indicated by the voltages $(V_p)_i$ and $(V_p)_o$.

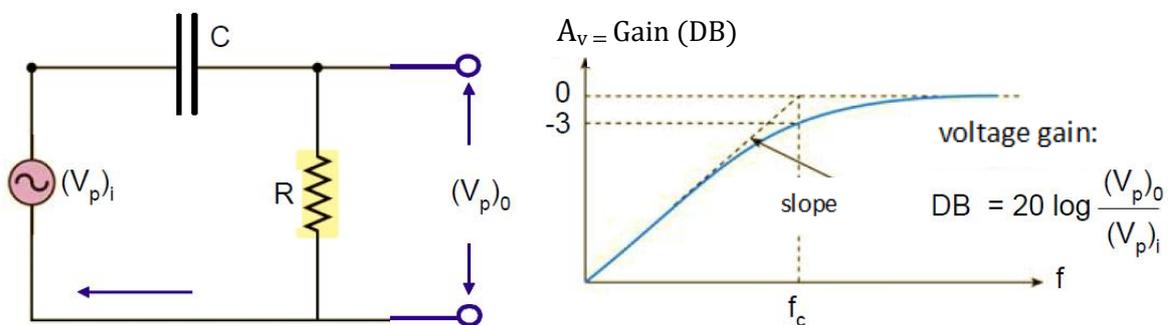


Figure 2. High frequency RC filter and Bode diagram

$$\omega_c = \frac{1}{CR} \quad f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi RC}$$

For an RC circuit to be used as a high-frequency filter, the output voltage must be taken at the terminals of resistor R. The peak (maximum) current in this circuit,

EEE 2006 CIRCUITS II LABORATORY

$$I_p = \frac{(V_p)_i}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}}$$

Since the voltage drop across the resistor is in phase with the current,

$$I_p = \frac{(V_p)_0}{R}$$

is. The ratio of the peak output voltage to the peak input voltage is found by dividing the first equation by the second and rearranging.

$$\frac{(V_p)_0}{(V_p)_i} = \frac{R}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{1}{\omega RC}\right)^2}}$$

$$V_{\text{çıkış,rms}} = V_{\text{rms}} \frac{R}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} = V_{\text{rms}} \frac{1}{\sqrt{1 + \left(\frac{1}{\omega RC}\right)^2}}$$

Low-Frequency RC Filters

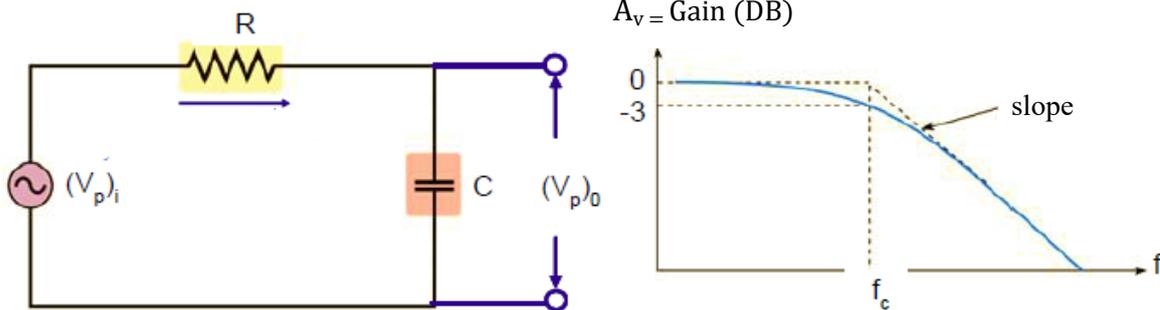


Figure 3.Low frequency RC filter and Bode diagram

For the low-frequency filter shown in Figure 3,

$$(V_p)_0 = I_p X_c = \frac{I_p}{\omega C}$$

$$\frac{(V_p)_0}{(V_p)_i} = \frac{1}{\omega C \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} = \frac{1}{\sqrt{1 + (\omega CR)^2}}$$

$$V_{\text{çıkış,rms}} = V_{\text{rms}} = \frac{1}{\omega C} V_{\text{rms}} \frac{1}{\sqrt{1 + (\omega CR)^2}}$$

RL Filters

RL circuits can also be used as filters. In these, the potential between the terminals of the reactive element is used for high-frequency filters and the potential between the terminals of the resistor for low-frequency filters. The behavior of these filters is the opposite of RC circuits. Low- and high-frequency filters are very important in the design of electronic circuits.



EEE 2006 CIRCUITS II LABORATORY

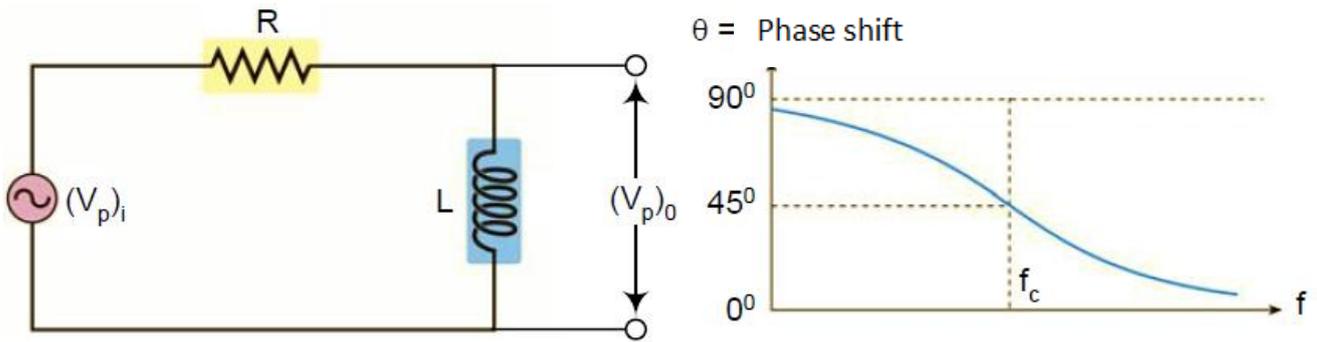


Figure 4. High frequency RL filter circuit

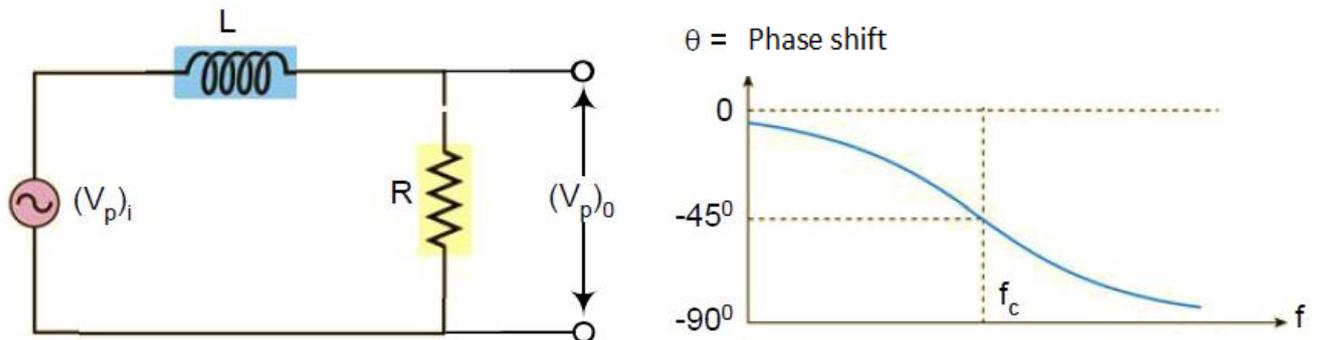


Figure 5. Low frequency RL filter circuit

$$\omega_c = \frac{R}{L} \quad f_c = \frac{\omega_c}{2\pi} = \frac{R}{2\pi L}$$

The frequency at which the output voltage is 0.7 times the input voltage is called the corner frequency (f_c). At this frequency, the phase shift between output and input is 45° .

Expressions of corner frequencies of RC and RL filters:

$$f_c = \frac{1}{2\pi RC}, \quad f_c = \frac{R}{2\pi L}$$

is calculated as.

EXPERIMENTS

Components Used in the Experiment

- Circuit module, Signal generator, A measuring instrument that can measure in the range of 20 mA AC and 20 V AC, Oscilloscope, Connection elements.
- 2 pcs 1 kΩ resistors
- 22 nF, 47 nF and 100 nF capacitors
- 68 mH, 100 mH and 10 mH inductances.

1. RESISTANCE-CAPACITANCE FILTER CIRCUITS

Purpose of the Experiment

- To learn the working principle of low-pass and high-pass filter circuits consisting of resistance and capacitance elements.
- To make a low-pass and high-pass filter circuit consisting of resistance and capacitance elements.
- Calculating the corner frequency using experimental measurements.



EEE 2006 CIRCUITS II LABORATORY

- To examine the frequency dependent changes of the output voltages of filters consisting of R and C elements.

Conducting Experiments

Experiment 1.1.

The experimental connection diagram of the low-pass filter circuit made of resistor and capacitance elements is given in Figure 6.

- Set up the circuit as shown in Figure 6.
- On the oscilloscope, Ch. 1 input voltage and Ch. 2 output voltage on the oscilloscope.
- Measure and adjust the output of the signal generator on an oscilloscope to obtain a sinusoidal voltage (V_i) of 6 volts peak-to-peak at the input of the circuit.
- Apply a sinusoidal voltage of 6 volts peak-to-peak to the input of the circuit and observe the output voltage V_0 for 100Hz, 1kHz, 10kHz, 100kHz values of the frequency from Ch 2 on the oscilloscope and record the measured values in Table 1.
- Ch. Adjust the frequency so that the amplitude of the signal in Ch. 2 is 0.7 times the input. Record the frequency you find in Table 1. This value is the corner frequency of the circuit.
- Measure the phase shift between the signal at Ch 1 (input voltage) and the signal at Ch 2 (output voltage) for 100Hz, corner frequency, 100kHz. Record the values obtained in Table 1.

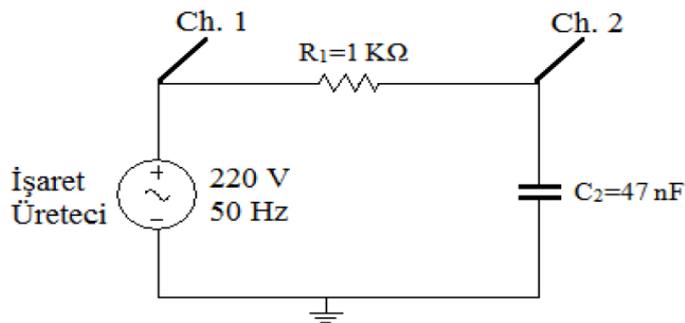


Figure 6. R-C low-pass filter circuit.

Table 1. Measurement results of R-C low-pass filter experiment

Frequency	100 Hz	1 kHz		10 kHz	100 kHz	Components
Input (Volt)	6	6	6	6	6	R=1 kΩ C=47 nF Low pass
Output (Volt)			4.2			
Phase Difference						

Experiment 1.2.

Change the positions of R and C elements in Figure 6. In this case the circuit will be a High Pass Filter. Repeat the same process and record the values in Table 2.

Table 2. Measurement results of R-C high-pass filter experiment

Frequency	100 Hz	1 kHz		10 kHz	100 kHz	Components
Input(Volt)	6	6	6	6	6	R=1kΩ C=47nF Low pass
Output (Volt)			4.2			
Phase Difference						



EEE 2006 CIRCUITS II LABORATORY

Draw the characteristics of R-C low-pass and high-pass filters on the axes in Figure 7 below.

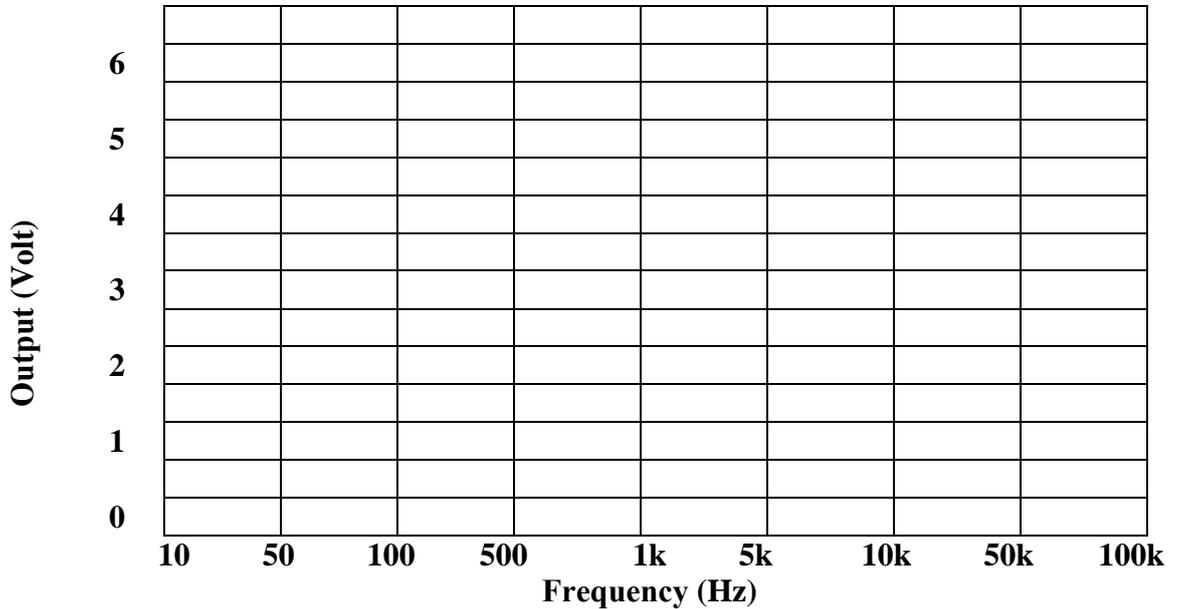


Figure 7. Experimental characteristics of R-C low-pass and high-pass filters.

Experiment 1.3.

Turn the circuit back into a low-pass filter and repeat the experiment for $R= 1\text{ k}\Omega$, $C=100\text{ nF}$, $R= 1\text{ k}\Omega$, $C=22\text{ nF}$ and $R= 2\text{ k}\Omega$, $C=22\text{ nF}$ and record the measured values in Table 3.

Table 3. Low-pass filter test measurement results for different R-C values

Frequency	100 Hz	1 kHz		10 kHz	100 kHz	Components
Input (Volt)	6	6	6	6	6	R=1 kΩ C=100 nF Low pass
Output(Volt)			4.2			
Input(Volt)	6	6	6	6	6	R=1 kΩ C=22 nF Low pass
Output(Volt)			4.2			
Input(Volt)	6	6	6	6	6	R=2 kΩ C=22 nF Low pass
Output (Volt)			4.2			

Draw the characteristics of the low-pass filter consisting of different R-C values on the axes in Figure 8 below.

EEE 2006 CIRCUITS II LABORATORY

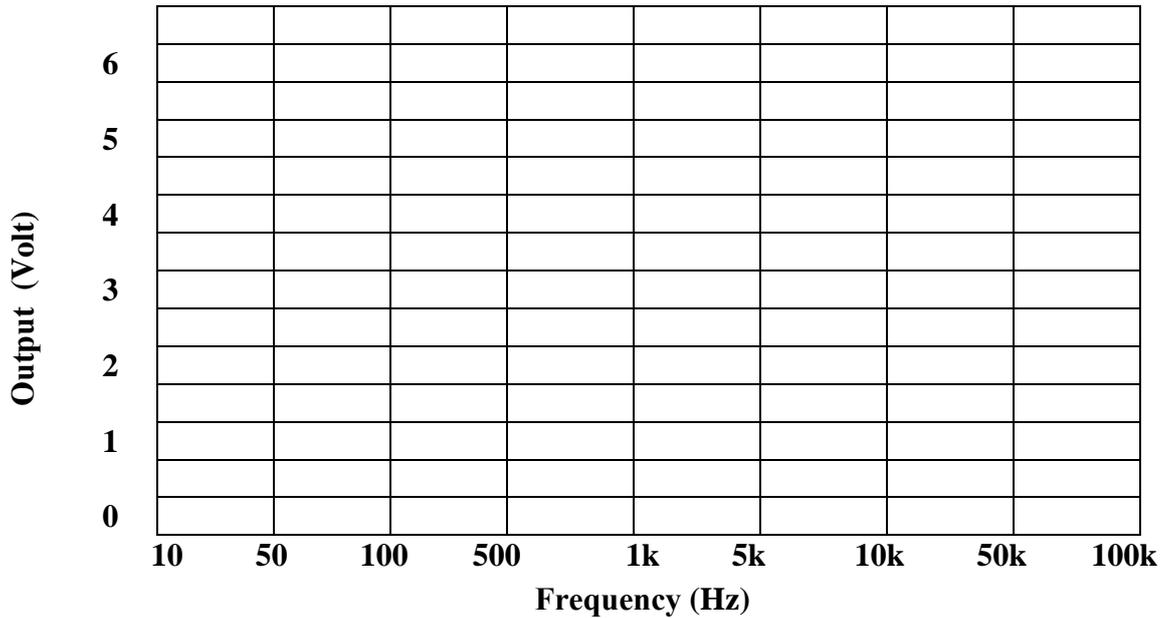


Figure 8. Experimental characteristics of the low-pass filter for different R-C values.

2. RESISTANCE-INDUCTANCE FILTER CIRCUITS

Purpose of the Experiment

- To learn the working principle of low-pass and high-pass filter circuits consisting of resistance and inductance elements
- To make a low-pass and high-pass filter circuit consisting of resistance and inductance elements
- Calculating the corner frequency using experimental measurements.
- To investigate the frequency dependent changes of the output voltages of filters consisting of R and L elements

Conducting the Experiments

Experiment 2.1.

The experimental connection diagram of the high-pass filter circuit made of resistance and inductance elements is given in Figure 9.

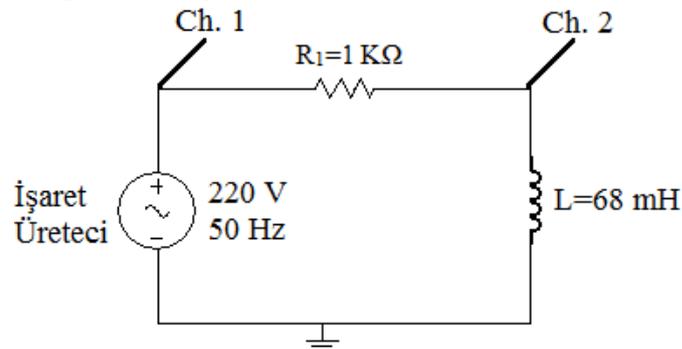


Figure 9. R-L high-pass filter circuit.



EEE 2006 CIRCUITS II LABORATORY

1. Set up the circuit as shown in Figure 9.
2. On the oscilloscope, Ch. 1 input voltage and Ch. 2 output voltage on the oscilloscope.
3. Adjust the output of the signal generator by measuring it on an oscilloscope to obtain a sinusoidal voltage (V_i) of 6 volts peak to peak at the input of the circuit.
4. Apply a sinusoidal voltage of 6 volts peak-to-peak to the input of the circuit and observe the output voltage V_0 for 100Hz, 1kHz, 10kHz, 100kHz values of the frequency from Ch 2 on the oscilloscope and record the measured values in Table 4.
5. Ch. Adjust the frequency so that the amplitude of the signal in Ch. 2 is 0.7 times the input. Record the frequency you find in Table 1. This value is the corner frequency of the circuit.
6. Measure the phase shift between the signal at Ch 1 (input voltage) and the signal at Ch 2 (output voltage) for 100Hz, corner frequency, 100kHz.

Table 4. Measurement results of R-L high-pass filter experiment

Frequency	100 Hz	1 kHz		10 kHz	100 kHz	Components
Input (Volt)	6	6	6	6	6	R=1 kΩ L=68 mH High Pass
Output (Volt)			4.2			
Phase Difference						

Experiment 2.2.

Change the positions of R and L elements in Figure 9. In this case the circuit will be a Low Pass Filter. Repeat the same process and record the values you find in Table.5.

Table 5. Measurement results of R-L low-pass filter experiment

Frequency	100 Hz	1 kHz		10 kHz	100 kHz	Components
Input (Volt)	6	6	6	6	6	R=1 kΩ L=68 mH Low Pass
Output(Volt)			4.2			
Phase Difference						

Draw the characteristics of R-L low-pass and high-pass filters on the axes in Figure 10 below.

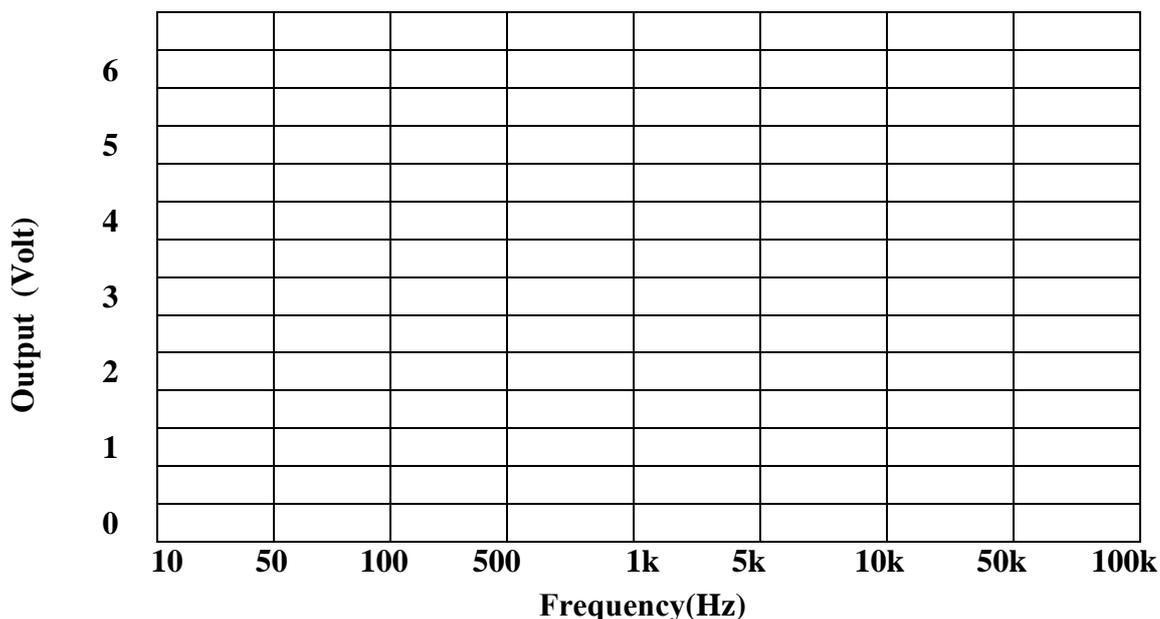


Figure 10. Experimental characteristics of R-L low-pass and high-pass filters.



EEE 2006 CIRCUITS II LABORATORY

Experiment 2.3.

Turn the circuit back into a high-pass filter and repeat the experiment for $R=2\text{ k}\Omega$, $L=68\text{ mH}$ and $R=1\text{ k}\Omega$, $L=136\text{ mH}$ and record the measured values in Table 6.

Table 6. Measurement results of high-pass filter experiment for different R-L values.

Frequency	100 Hz	1 kHz		10 kHz	100 kHz	Components
Input (Volt)	6	6	6	6	6	R=2 k Ω L=68 mH High pass
Output (Volt)			4.2			
Input (Volt)	6	6	6	6	6	R=1 k Ω L=136 mH High pass
Output(Volt)			4.2			

Draw the characteristics of the high-pass filter consisting of different R-L values on the axes in Figure 11 below.

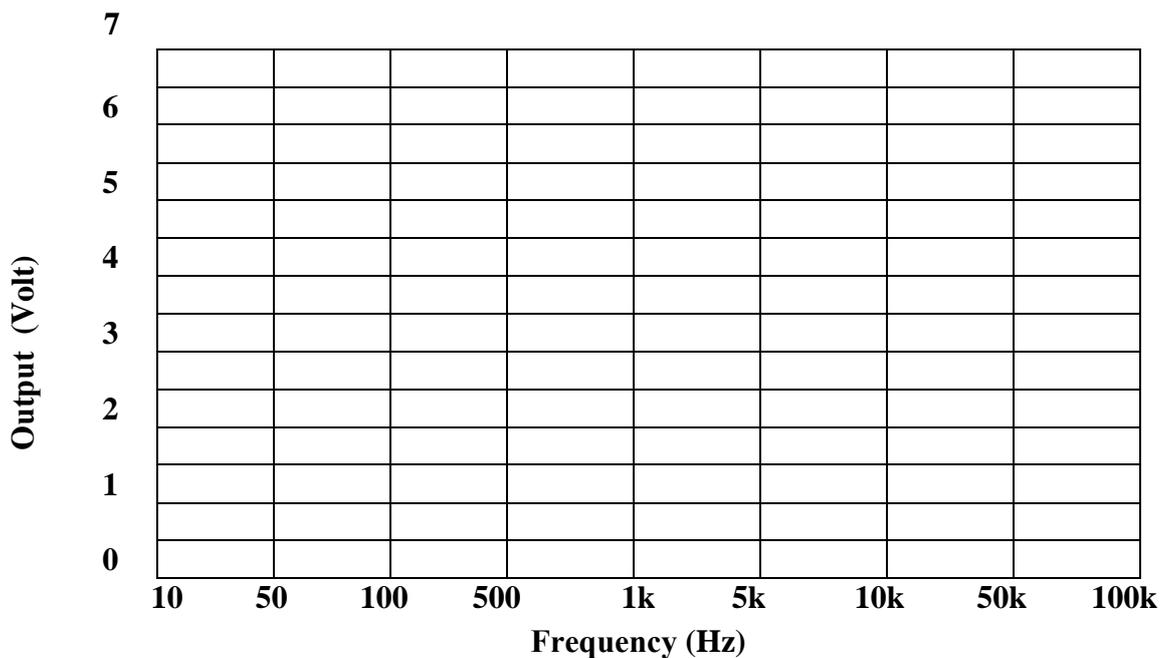


Figure 11. Experimental characteristics of the high-pass filter for different R-L values.

IMPORTANT NOTE

In order to perform the experiments properly, preparatory questions should be done and the theoretical part of the methods should be well known.