


Number:
 Name Surname:
 Department:

3. WHEATSTONE BRIDGE

The Purpose of the Experiment: Finding unknown resistors by using Wheatstone Bridge.

Theoretical Background:

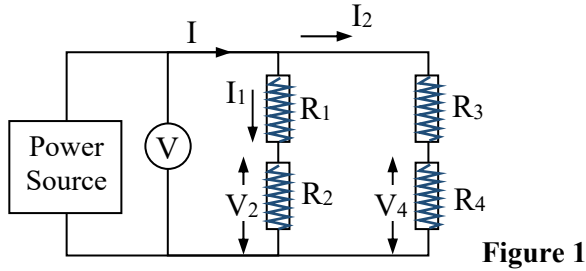In the circuit in Figure 1, the currents passing through the branches are



$$I = I_1 + I_2$$

$$I_1 = \frac{V}{R_1 + R_2}, I_2 = \frac{V}{R_3 + R_4}$$

Here, the voltages of the resistors R_2 and R_4 are

$$V_2 = I_1 R_2 = \frac{VR_2}{R_1 + R_2}, V_4 = I_2 R_4 = \frac{VR_4}{R_3 + R_4}$$

and the difference of these voltages is

$$\Delta V = V_2 - V_4 = V \left(\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right)$$

Condition $\Delta V = 0$ is independent of V , and the balance condition of the bridge is expressed by

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

*** CAUTION ***

During the experiment, set the multimeter indicated with the letter V on it as a Voltmeter at 20V and the multimeter indicated with the letter A as an Ammeter at 200mA. Use the devices at this stage during the entire experiment. DO NOT CHANGE.

Experiment:

- i. Set up the circuit in Figure 2 and adjust the voltage from the power supply to 10 V, read the voltages from the voltmeter for the lengths $x = 5, 15, 25, 35, 45$ cm and write them in Table 1. (When setting up the circuit, connect the negative end of the power supply to the zero meter on the resistor bar.!)
- ii. By drawing the graph $V(x)$, observe whether the voltage changes proportionally with the distance x on the resistor bar.
- iii. Set up the circuit in Figure 3.
- iv. For the 4, 6, 8, 10 V values, respectively, read the lengths of a and b in cases where the bridge provides the equilibrium state (the Ammeter shows zero!) and record them in Table 2.
- v. By using the a and b values you determined, find the unknown resistance R_x in the expression

$$\frac{a}{b} = \frac{R_3}{R_x}.$$

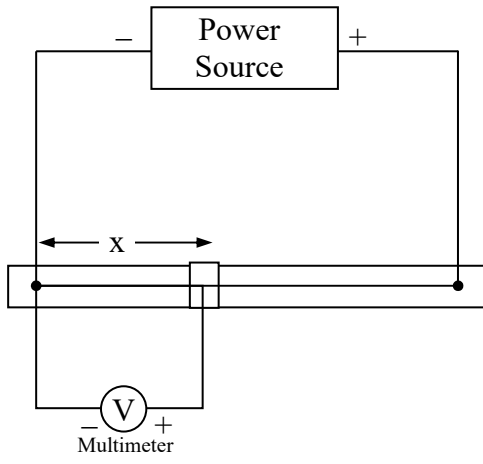


Figure 2

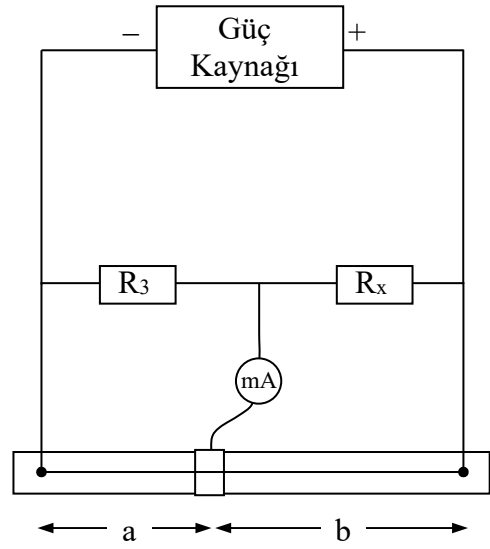


Figure 3

Table 1					
x (cm)	5	15	25	35	45
V (V)					

Table 2.

V (V)	a/b	R_x (Ω)
4		
6		
8		
10		

Comment: